

**DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
UNIVERSITY OF BRITISH COLUMBIA
CPEN 211 Introduction to Microcomputers, Fall 2017
Lab 5: Datapath of the “Simple RISC Machine”**

L1E: handin deadline is 7:59 PM Oct 11; Demos are on Oct 12th

L1C: handin deadline is 7:59 PM Oct 12; Demos are on Oct 13th

L1A, L1B, L1D: handin deadline is 7:59 PM Oct 16; Demos are on Oct 17th

All sections: Lab 6 due the week of Oct 23-27

1 Introduction

Labs 5 through 8 provide a bridge between the first and second half of CPEN 211. Starting with this lab and continuing in the next three you will build a computer that implements a “Reduced Instruction Set Computer” (RISC). The chips that power iPhone and Android smartphones also include a computer using a RISC “instruction set architecture” (ISA) known as ARM. By completing this series of lab you will have key insights into how those chips work. Labs 5 through 8 develop foundational knowledge you will use when we learn how to program ARM chips in “assembly” code later in CPEN 211. Assembly code is the level of software that is “closest” to the hardware.

WARNING: You may find yourself spending a significant amount of time tracking down bugs during Lab 5 to 8. If this happens you should review the “debugging video” <https://youtu.be/2c3CZouKJKs>.

1.1 From C to Assembly

The “Simple RISC Machine” executes programs written using a *very* small set of “instructions”. Instructions are the smallest unit of computation that a programmer can specify. Section 8 at the end of this handout provides a complete list of the instructions your computer will execute at end of Lab 8. This set of instructions is “Turing-complete” meaning your Simple RISC Machine computer could in principle run any program given enough time and enough memory.

To start, consider the following line of C code:

```
f = (g + h) - (i + j);
```

To execute this C code on the Simple RISC Machine architecture we will see it is necessary for a compiler—or CPEN 211 student—to first divide the computation into three separate “instructions”. Each of the three instructions will specify a small portion of the above computation. These steps are analogous to steps in a cookbook recipe. For example, to bake bread you might follow the steps: “1. Mix flour, water and yeast; 2. Let dough rise; 3. Bake in oven.” Similarly, we can implement the C code above using the following three Simple RISC Machine (SRM) instructions:

```
ADD t1, g, h;  
ADD t2, i, j;  
SUB f, t1, t2;
```

The first instruction, “ADD t1, g, h”, adds the value of the variables “g” and “h” and puts them into the *temporary variable* “t1”. You probably noticed that “t1” was not a part of our original C program. We used this temporary variable to help us split up our long line of C code into smaller steps. Similarly, the second line adds the variables “i” and “j”. Finally, the third line subtracts the temporary variable t2 from t1 and puts the result in f. You should understand *why* these instructions compute the same value for f as the C code above.

To implement a computer that can execute these instructions we will need a block of hardware that can add and subtract numbers. We also need some hardware that can store the numbers before and after the addition and subtraction operations. The following section describes one hardware design for a computer that can execute ADD and SUB instructions like those above.

1.2 Overview of the Simple RISC Machine Datapath

To execute the instructions above along with some others described later, in Lab 5, you implement the computer *datapath* shown in Figure 1. This section explains the different elements in Figure 1. While reading this section try to focus on understanding what each individual block does. In Section 2 we will see an example showing how the blocks work together.

The datapath consists of one register file ① containing 8 registers, each holding 16-bits; three multiplexers ⑥⑦⑨; three 16-bit registers with load enable ③④⑤; a 1-bit register with load enable ⑩; a shifter unit ⑧; and an arithmetic logic unit (ALU) ②. Below we describe each component in detail.

1.2.1 Register File

To compute with the variables *g*, *h*, *i*, *j*, *t1*, and *t2*, our computer needs a way to “remember” their values. To remember their values, the Simple RISC Machine employs the hardware structure known as a *register file* ①, shown in Figure 1.

A register file is a small memory. A *memory* is a hardware block that remembers information. It does this by storing the information as numbers consisting of a fixed number of bits in a fixed number of *locations*. Each location has associated with it an *address*. The address of a memory location is analogous to the street address of a house. The address identifies the house, but is distinct from the contents of the house (who lives there). Another analogy is looking for a book in a library: Each book in a library has a “call number”. The call number helps you find the book inside the library. In this analogy, the call number acts like a memory address and the text inside of the book acts like the data (i.e., numbers) that we store in a memory location. For example, suppose we save the number 42 in memory location with address 3. Later we can ask the memory for the contents at address 3 and the memory will return the value 42. In most computers each memory location holds an 8-bit quantity known as a byte. Some memories have a large number of locations so they can store lots of information. For example, if your computer or phone has 16 GB of RAM, this means it has 16 billion locations (the “G” means giga, which stands for one billion), each of which stores an 8-bit value, also known as a *byte* of information (byte is abbreviated to “B”). To simplify the overall design, in the Simple RISC Machine, each location will hold 16-bits.

The register file for the Simple RISC Machine is a memory that has eight locations numbered 0 through 7, each of which can hold a 16-bit number. Notice that to specify one of the eight locations requires only $\log_2(8) = 3$ -bits, even though each location can hold 16-bits. The eight different locations are more commonly referred to as *R0*, *R1*, ..., *R7*, where the *R* stands for “register”. Thus, the entire register file can store $8 \times 16 = 128$ bits of information. An *individual* 16-bit register inside the register file is built using what is sometimes referred to as a *register with load enable*. A register with load enable can be implemented with the circuit shown in Figure 2, which you should know how to build based upon the material you will have seen in lecture by the time we reach the end of Slide Set 5 in lecture on Tuesday Oct 3.

In Figure 2, when *load* is 0, *out* is passed through the top input of the multiplexer into the *D* input of the set of 16 flip-flops, which together form a 16-bit register. Thus, when *load* is 0 and there is a rising edge of the clock, the value in the 16-bit register does *not* change. Conversely, when *load* is 1 the value of *out* is updated to the value on *in* on the rising edge of the clock. In Figure 1 a 16-bit register with load enable is represented using the symbol shown in Figure 3.

To implement the register file, you will use eight separate instances of the 16-bit register with load enable circuit. The overall logic diagram for the complete register file is shown in Figure 4. You will notice this diagram includes two *decoder* blocks. A decoder is a combinational logic circuit which you will learn about when we cover the start of Slide Set 6, which we will either be Tuesday Oct 3 or the pre-recorded lecture for Thursday Oct 5th. To keep it readable, Figure 4 does not show all locations (e.g., *R4*, *R5* and *R6* are omitted).

To store the value of a variable into the register file, we need to pick one of the eight 16-bit registers with load enable. In APSC 160 this choice was made for you by your C compiler. In CPEN 211 you will

 


Figure 1: "Simple RISC Machine" Datapath

 


Figure 2: Register with Load Enable Circuit

need to make this choice yourself. For example, we could decide that for our example program we will put "g" in R0, "h" in R1, "i" in R2, and "j" in R3. Thus, our program now looks like:

```
ADD t1, R0, R1;
ADD t2, R2, R3;
SUB f, t1, t2;
```

Now, for this example you still need to allocate registers in the register file for t1, t2 and f. Let's use R4 and R5 to hold t1 and t2. What about "f"? Well, you could use R6, but you are starting to run very low on "free" registers. If the program contains only the one line of C code it does not need to hold onto "g" after the first instruction so you can reuse R0 for "f". After making these register "allocation decisions" the program looks like the following:

```
ADD R4, R0, R1;
ADD R5, R2, R3;
SUB R0, R4, R5;
```

Now, let's consider how the value of variable "j" gets into and out of R3 inside the register file.

 


Figure 3: Register with Load Enable Symbol (Note: this symbol is used in both Figure 1 and 4)

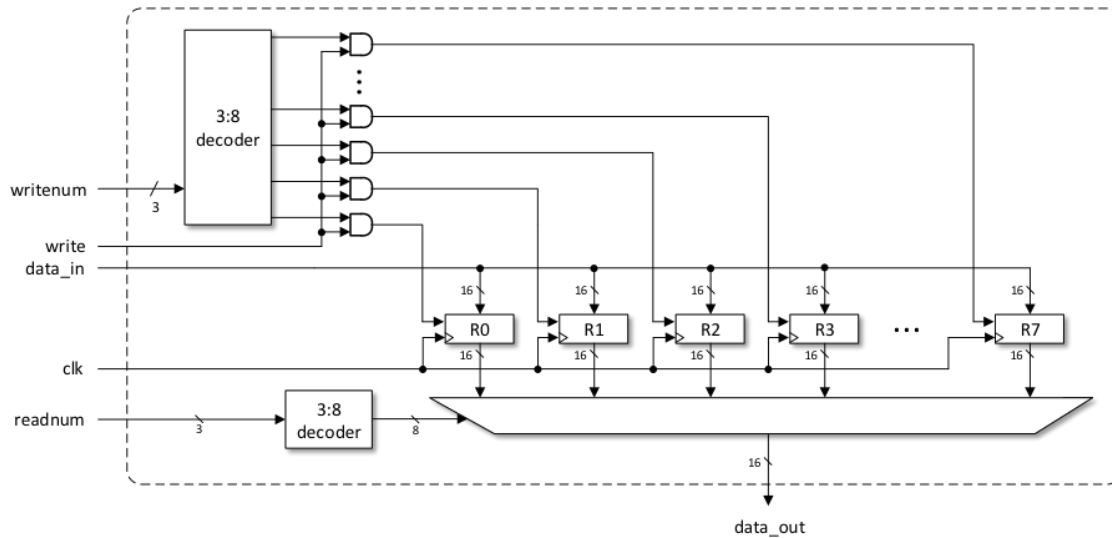


Figure 4: Register File Internal Structure

Suppose we want “j” to have the value 42 *before* we start executing our code. To put 42 in R3 you would place the 16-bit value 000000000101010 (binary for 42) on `data_in`, set the 3-bit input `writenum` to 011 (binary for 3), set `write` to 1 to indicate we wish to save, or *write*, the value 42 into location 3 in the register file, and input a rising edge on `clk`. This causes, the output of the upper 3:8 decoder to be driven to 00001000. Each output bit of the decoder is AND’ed with `write`. As `write` is 1, the load input to R3 is set to 1. On the rising edge of `clk` 000000000101010 will be copied to the 16-bit Q output of R3. At most one load enable input to R0 through R7 will be 1. If `write` is 0 all 8 load-enable signals are 0. Section 2 describes in more detail the “MOV” instruction that is used to write a constant into a register using the above steps.

To recall, or *read*, the value of “j”, which is now stored in R3, we set the 3-bit bus `readnum` to 011. The 8-bit output of the lower 3:8 decoder will be 00001000 and this will cause the 8-input one-hot select mux to copy the value of R3 to `data_out`.

This register file is said to have two *ports*: one *write* port and one *read* port. Thus, up to one write and one read can be performed simultaneously. The read is combinational: whenever `readnum` changes, the value from the indicated register is driven out of the register file after some combinational delay. **THE REGISTER READS ARE NOT COORDINATED TO THE CLOCK!** The register write, however, is coordinated to the clock. At each rising clock edge, if `write` is 1, the value on the 16-bit register file input `data_in` is written into the register indicated by the value on `writenum`. This write only happens on the rising clock edge. If, at the clock edge, `write` is 0, no register is updated. Be sure you follow the Verilog style guidelines for your register file code.

Value on ALUop input	Operation
00	Ain + Bin
01	Ain - Bin
10	Ain & Bin
11	~Bin

Table 1: ALU operations

shift	Operation
00	B
01	B shifted left 1-bit, least significant bit is zero
10	B shifted right 1-bit, most significant bit, MSB, is 0
11	B shifted right 1-bit, MSB is copy of B[15]

Table 2: Shift Operation Encoding

1.2.2 Arithmetic Logic Unit

This funny symbol labeled ②, which is a trapezoid with a little triangular notch, represents an *arithmetic logic unit* (ALU). The ALU can perform arithmetic or logical operations. This is the main piece of hardware that actual “computes” things inside a computer. Which operation should be performed by your ALU is indicated by the value on the ALUop input shown in Table 1.

Note that it is important you use the values in the above table or in Lab 7 and 8 the assembler program we give you will generate code that does not work with your Simple RISC Machine. Your ALU should be purely combinational (there is no clock input). Whenever one of the inputs or ALUop lines change, the output changes appropriately (the Verilog “+” and “-” operations are combinational).

1.2.3 Pipeline Registers

The datapath contains three 16-bit registers ③④⑤ with load enable that are not included in the register file. These hold the datapath signals A, B, and C. We will use these registers while executing an individual instruction. We need at least one of the two registers A and B because the ALU is purely combinational and the register file can read out only one of R0 through R7 at a time. You may want to try to eliminate the other two registers in Lab 8 but for now you should keep them.

1.2.4 Source Operand Multiplexers

To enable more complex instructions besides addition and subtraction it is helpful if we can change the inputs to the ALU via the source operand multiplexers ⑥⑦. For some instructions added in Lab 6 through 8 these multiplexers are used to set the 16-bit Ain input to the ALU to zero. For other instructions we use them to input an “immediate operand” (described in Lab 6).

1.2.5 Shifter Unit

Some instructions are made more powerful with the ability to quickly multiply one of the inputs to the ALU by a power of 2 or perform integer divide by a power of 2. The shifter unit ⑧ is a purely combinational logic block that accomplishes this as follows. The shifter takes one 16-bit input from the Q output of register B ⑦ and outputs either the same value or the value shifted one bit to the left or right according the value on “shift” as described in Table 2.

For example, if the input to the shifter was 1111000011001111, then the output of the shifter would be as shown in Table 3.

shift	Output of shifter
00	1111000011001111
01	1110000110011110
10	0111100001100111
11	1111100001100111

Table 3: Example shift operations starting with 1111000011001111

1.2.6 Writeback Multiplexer

Once the ALU has computed a value the main 16-bit result is captured in register C. If we want to use this value as the input to a subsequent instruction we need to write it into the register file. However, we will also want to input values into the register file from other sources. Thus, we add a writeback multiplexer 9.

1.2.7 Status Register

In Lab 8 we will add support for instructions used to implement features of C such as “if” statements. These instructions will need to know some information about the values being computed up to that point in the program. One important piece of information will be if the main 16-bit result of the ALU was exactly zero. If so, the status register 10 will be set to 1 otherwise it will be set to 0.

2 Example Datapath Operation

Consider the addition of two registers, R2 and R3 with the result being stored in R5. The addition takes four clock cycles. During the first cycle, readnum is set to 2 to indicate we want to read the 16-bit contents of R2 from the register file. At the same time loada is set to 1 to indicate that register A should be updated on the next rising edge of the clock (note the little triangle in the bottom left of register A indicates a clock input). During the second cycle, we set loada back to 0, set readnum to 3 to indicate we now want to read the 16-bit contents of R3. At the same time loadb is set to 1. With these control input settings on the next rising edge of the clock the contents of R3 will be copied to register B. During the third cycle loadb is set back to 0, ALUop is set to “00” to indicate addition (see Table 1 above), asel is set to zero to ensure the value in register A appears at the Ain input to the ALU. Similarly, bsel is set to 0 to indicate the output of the shifter unit appears at the Bin input to the ALU. The shifter unit is combinational logic that takes the 16-bit contents of B as its input and outputs the value either unmodified, or shifted to the left or right by one bit position depending upon the control input “shift”. During this cycle the shift input is set to “00” to indicate the value in B should not be shifted. Also during this cycle, loadc is set to 1 to ensure the result of the addition is saved in register C on the next rising edge of the clock. We can optionally set loads to 1 if we want to record the “status” of the computation. In this lab the status will simply indicate if the 16-bit result of the ALU was zero. In later labs we will see how this status information can be used to help implement “if” statements and “for” loops in a language like C or Java. During the fourth cycle, loadc is set back to 0, vsel is set to 0, write is set to 1, and writenum is set to 5. Together these cause the value in register C to be fed back and written into register R5 within the register file.

Note that during the fourth cycle, the value fed back also appears on the output pins datapath_out. For this lab you can connect datapath_out to the 7-segment displays on the DE1-SoC using the logic provided in lab5_top.v. This will be the primary way to tell if your datapath is working when it is on the DE1-SoC. However, this is not the fastest or easiest way to debug your circuit.

As alluded to earlier, the basic interface between hardware and software inside a computer is through “instructions”. Each instruction tells the computer how to move and operate upon some data. Consider an instruction of the form “MOV R2, #32”. This instruction would load the actual number 32 into register R2. This can be performed with the datapath as follows:

During the first cycle, assume the number 32 appears on the 8-bit signal datapath_in (in a later lab,

we will consider more realistic memory read/write strategies). During this same cycle, `vsel` is set to 1, `write` is set to 1, and the number 2 (indicating register #2) is driven on `writenum`. Note that this instruction can be performed in only one cycle, unlike the `ADD` instruction, which takes 4 cycles. This will become important in the next assignment.

If you have trouble following the above discussion, please also review the slides “Lab 5 Introduction” on Piazza which will be briefly discussed during lecture on Oct 5 which will be pre-recorded from 5:30 to 7:30 pm on Oct 3 following the regular Tuesday lecture. Also, the following video shows your instructor demonstrating a working Lab 5 implementation using a DE1-SoC showing how executing instructions will look when you are done: https://courses.ece.ubc.ca/cpen211/2016/lab5_demo/lab5_demo.html.

3 Lab Procedure

You will get through the lab far more quickly if you break down the overall work into smaller parts and complete, compile and test (using a testbench) each one *before* moving on to the next. If you are worried you will not have time to do the entire lab then see the marking guideline in Section 4 to see how you can earn part marks.

3.1 Revision Control and Regression Tests

Whether you work alone or with a partner, you will save time if you learn to use a revision control system such as “git”. There are many tutorials on how to use “git” online. E.g., <https://www.atlassian.com/git/tutorials>, <https://try.github.io/levels/1/challenges/1>. Using a revision control system is standard industry practice and more effective than emailing files between partners. Use a (free) **private** online repository such as <https://bitbucket.org> or <https://education.github.com>. However you collaborate with your partner it is your responsibility to make sure it is secure and private so no other students in CPEN 211 or at other schools see your code. Revision control goes “hand in hand” with a great engineering practice known as “regression testing”. Briefly, the idea of regression testing is that, any time you change something you re-run all of your testbenches. Regression testing can be fast if you make your testbenches “self checking” by printing out a “PASS/FAIL” message at the end of the simulation (see example in Slide Set 5). Every time you make a change to a given hardware unit (e.g., the register file or ALU), you rerun all your tests and only submit your changes to the revision control system if all your tests “pass”. To speed this up, run ModelSim from the command line. For example, for the starter code from Lab 3, create a new file “regress.do” containing:

```
vlib work
vlog tictactoe.v
vsim -c work.TestTic
run -all
quit -f
```

If using Notepad: File>Save As... and for “File Name” enter, **including double-quotes**, “regress.do”, then press “Save”. Then, launch “cmd.exe” and at the C:\ prompt type `cd <dir>` replacing `<dir>` with the directory containing “regress.do” and “tictactoe.v”. Then, type `vsim -c -do regress.do` and hit enter. You should see outputs like you would in the transcript window in ModelSim.

3.1.1 Recommended Development Sequence

You may divide up the work between partners but both students must understand the complete design well enough to code any part of it as you may be asked to write similar code on a lab proficiency test.

1. Create a new ModelSim project called lab5.
2. Add a file `regfile.v` and write synthesizable code for your register file in this file. Note that this Verilog must conform to the style guidelines. Compile `regfile.v` in ModelSim to catch syntax errors.
3. Add a file `regfile_tb.v` to your project for your register file testbench module. Section 8 provides some tips on how to write good unit level testbenches and introduces some Verilog syntax for

automatically checking if the output results are correct to enable what is known as regression testing.

4. Compile and simulate `regfile_tb.v` along with `regfile.v` in ModelSim. Remember to use the waveform viewer. Even if everything looks OK add some internal signals from inside the register file module you defined in `regfile.v` to your waveform viewer and rerun the simulation to verify the internal operation is as you expect.
5. Debugging. In the very likely case that a signal (wire or reg) appears wrong in the waveform viewer, first find the Verilog corresponding to the hardware block that “drives” that signal. If there is an obvious error in the code for that block that can explain the exact wrong result you are seeing, then try fixing it. If there is no obvious error then you should not change the Verilog for that block! If you do make a change, remember to recompile your Verilog, restart the simulation and rerun the simulation. If your change did not fix the specific bug you were trying to fix, then undo it! This is important! If you make changes to your code that do not fix the bug they tend to make it harder to find the bug you were original interested in because the bug tends to “move around”. Instead of “undo” you can also comment out the “fix” code you added so you can get it back quickly in case you do end up needing it. Now, if/when you run out of things that could be wrong with the block defining the signal that looks wrong, do your best to guess which inputs to that block could lead to this incorrect output. Then add all the input signals to the block to the waveform viewer and restart the simulation and rerun it. If one of those inputs seems wrong, repeat Step 5 starting with the block that drives that signal. See Section 7 for more debugging tips.
6. Once you are satisfied that your register file works in simulation, compile `regfile.v` in Quartus and verify you see no inferred latches warnings. After synthesis completes, view the resulting logic diagram schematic that Quartus generates using “Tools” > “Netlist Viewers” > “RTL Viewer” to verify the hardware looks as you expect (e.g., combinational logic or flip-flops).
7. (Optional) Download the register file to your DE1-SoC and connect it to some top level signals. This step is time consuming. Do this step only if you have time or encounter bugs in Step 13.
8. Only after you have debugged the register file should you go through Steps 2-6 for the ALU.
9. Only after you have debugged the ALU should you go through Steps 2-6 for the shifter.
10. Now that all three main datapath modules are trusted to work, instantiate them in your datapath and add the remaining building blocks. Instantiate each of the three units (Register file ①, ALU ② and Shifter ⑧) inside `datapath.v`. Then, add in the remaining logic blocks ③④⑤⑥⑦⑨⑩ to your datapath module using synthesizable Verilog that conforms to the style guidelines. Use no fewer than one always block or assign statement per hardware block in Figure 1. Register A, B, and C will each require an instantiated flip-flop module and an assign statement for the enable input in order to conform to the style guidelines.
11. Write a top level testbench for your datapath in `datapath_tb.v`. It should implement at least the sequence shown below:

<code>MOV R0, #7</code>	; this means, take the absolute number 7 and store it in R0
<code>MOV R1, #2</code>	; this means, take the absolute number 2 and store it in R1
<code>ADD R2, R1, R0, LSL#1</code>	; this means $R2 = R1 + (R0 \text{ shifted left by } 1) = 2 + 14 = 16$
12. Test the overall datapath in ModelSim. If you see any suspicious outputs you should follow the debugging procedure in (b) to find relevant internal signals to add to the waveform viewer and restart and rerun the simulation.

13. Only after your overall design is working in ModelSim should you compile your top level and attempt to download to your DE1-SoC. Use `lab5_top.v` ONLY to help with this step. If you encounter bugs here try step (d). If you still are not sure what is going on and why the results differ from ModelSim then modify `lab5_top.v` to connect internal signals within your datapath to the LEDs on your DE1-SoC to help you follow the debugging rule “Quit Thinking and Look”.

4 Marking Scheme

A reminder that *both* partners must be in attendance during the demo. Any partner who is absent will automatically receive a mark of zero even if they did their fair share of the work.

Your mark will be computed as the sum of the following. Partners may get a different mark based upon their ability to answer the TA's questions. If it becomes apparent one partner did more than two thirds of the work the partner who did less will receive a mark of zero. You **must** include at least one line of comments per always block, assign statement or module instantiation and in test benches you must include one line of comments per test case saying what the test is for and what the expected outcome is.

3 Marks One mark for each of `regfile.v`, `alu.v` and `shifter.v`. Up to half of the marks may be deducted here for violations of the style guidelines or for lack of comments.

3 Marks For each of the unit level testbenches for your ALU, shifter and the register file. To receive full marks you must test both basic functionality and some “corner cases”. A corner case is an input you are not expecting to see or not expecting to see often. You may lose up to 2 marks if your test cases are not commented (one line per test case saying what is being tested and the expected outcome).

1 Marks For your `datapath.v`. Your Verilog must both be completed and conform to the style guidelines to receive this mark. Again, marks will be deducted for violations of the style guidelines or for lack of comments.

1 Marks For your `datapath_tb.v`.

2 Marks Demonstrate your datapath works on your DE1-SoC using a test case of your own devising. Your TA will need to be convinced your design really works to get full marks. The following video should give you an idea how this part might look: https://courses.ece.ubc.ca/cpen211/2016/lab5_demo/lab5_demo.html. To ensure all students can be marked within the duration of your lab session your TAs will give you no more than 5 minutes to complete this part and may give you zero if you cannot complete the demo in this time. Both partners should be active participants in the demo (e.g., one partner does one step, another does the next). You should practice your demo to avoid losing marks.

5 Lab Submission

Remember the lab code including all files created by ModelSim and Quartus must be submitted by the deadline shown on Page 1 of this handout the day before your lab section using handin. Use the same procedure outlined at the end of the Lab 3 handout except that now you are submitting Lab 5, so use:

```
handin cpen211 Lab5-<section>
```

where <section> should be replaced by your lab section. Remember you can overwrite previous and trial submissions using -o, as follows:

```
handin -o cpen211 Lab5-<section>
```

6 Lab Demonstration Procedure

To reduce congestion in the lab we will be dividing each lab section into two one hour sessions. For example, for L1A the first session will run from 9 am to 10 am and the second session will run from 10 am to 11 am. We request that you show up no more than 10 minutes before the start of your assigned one hour “Lab5-Time”, which will be posted on Connect at least 24 hours before your lab section along with your “Lab5-TA”. The TAs will have a randomly ordered list of lab partners and will start working their way down the list marking. Look for “Lab5-Marking-Order” on Connect to get a rough idea. If you and your partner are not present when your TA asks to mark you, your name will be put to the end of the list. If this happens the TA will be under no obligation to mark you, but may do so at their own discretion and if there is remaining time before the end of the lab section. In addition, the TAs may use a timer to ensure fairness in the amount of time given to each student. Bring your DE1-SoC to your lab section. Your TA will have your submitted code at their “TA marking station”.

7 Debugging Tips

See the debugging video <https://youtu.be/2c3CZouKJKs> for details of how to trace a bug to its source. Some other tips and tricks that you may find helpful:

1. SystemVerilog assertions. If you save your testbench file with the extension .sv and set the file properties to SystemVerilog you can make your testbench “self checking” by using the SystemVerilog assert statement. If we expect “s” to be 3’b100 at some point during the test script then we could write:

```
assert (datapath_tb.DUT.MUX1.s == 3'b100) $display("PASS");
      else $error("FAIL");
```

If you want simulation to stop on an error go to “Simulate > Runtime Options...” then select the “Message Severity” tab and change the setting for “Break Severity” to “Error”.

2. The following Verilog “force” and “release” syntax can be helpful for debugging after you put your datapath together if you later find a bug. In ModelSim from a test script and using the above external name syntax you can override the logic value generated by the circuit itself to “inject” your own test values using the Verilog keyword “force”. Continuing the example above, suppose “s” has the value “010” but you would like to see what the output “b” of instance “m” is if instead “s” was “100”. You could write the following line in your Verilog testbench script to find out:

```
force datapath_tb.DUT.MUX1.s = 3'b100;
```

Later in your test script you can go back to using the value generated by the circuit by using “release”:

```
release datapath_tb.DUT.MUX1.s;
```

8 The Simple RISC Machine Instruction Set Architecture

The information in Table 4 and 5 is only relevant to Lab 6 through 8. Each row in these tables specifies a single instruction. The assembly syntax is in the leftmost column. Each instruction is encoded using 16-bits. The next 16 columns indicate the binary encoding for the instruction. The last column on the right summarizes the operation of the instruction. The most significant 3-bits of each instruction (bits 15 through 13) are the opcode which indicates which instruction or class of instruction is represented.

Terminology quick definitions. These will be explained in more detail in the Lab 6 to 8 handouts.

- Rn, Rd, Rm are 3-bit register number specifiers.
- im8 is an 8-bit immediate operand encoded as part of the instruction.
- im5 is a 5-bit immediate operand encoded as part of the instruction.

Assembly Syntax (see text)	“Simple RISC Machine” 16-bit encoding																Operation (see text)	
	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0		
Move Instructions	<i>opcode</i>			<i>op</i>		<i>3b</i>			<i>8b</i>									
MOV Rn, #<im8>	1	1	0	1	0	Rn			im8								R[Rn] = sx(im8)	
MOV Rd, Rm{, <sh_op>}	1	1	0	0	0	0	0	0	Rd	sh	Rm					R[Rd] = sh_Rm		
ALU Instructions	<i>opcode</i>			<i>ALUop</i>		<i>3b</i>			<i>3b</i>	<i>2b</i>	<i>3b</i>							
ADD Rd, Rn, Rm{, <sh_op>}	1	0	1	0	0	Rn			Rd	sh	Rm					R[Rd]=R[Rn]+sh_Rm		
CMP Rn, Rm{, <sh_op>}	1	0	1	0	1	Rn			0	0	0	sh	Rm					status=f(R[Rn]-sh_Rm)
AND Rd, Rn, Rm{, <sh_op>}	1	0	1	1	0	Rn			Rd	sh	Rm					R[Rd]=R[Rn]&sh_Rm		
MVN Rd, Rm{, <sh_op>}	1	0	1	1	1	0	0	0	Rd	sh	Rm					R[Rd]=~sh_Rm		
Memory Instructions	<i>opcode</i>			<i>ALUop</i>		<i>3b</i>			<i>3b</i>	<i>5b</i>								
LDR Rd, [Rn{, #<im5>}]	0	1	1	0	0	Rn			Rd	im5							R[Rd]=M[R[Rn]+sx(im5)]	
STR Rd, [Rn{, #<im5>}]	1	0	0	0	0	Rn			Rd	im5							M[R[Rn]+sx(im5)]=R[Rd]	

Table 4: Instructions you will add in Lab 6

Assembly Syntax (see text)	“Simple RISC Machine” 16-bit encoding																Operation (see text)
	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
Branch	<i>opcode</i>			<i>cond</i>					<i>8b</i>								
B <label>	0	0	1	0	0	0	0	0	im8								PC+=sx(im8)
BEQ <label>	0	0	1	0	0	0	0	1	im8								if Z=1 then PC+=sx(im8)
BNE <label>	0	0	1	0	0	0	1	0	im8								if Z=0 then PC+=sx(im8)
BLT <label>	0	0	1	0	0	0	1	1	im8								if N!=V then PC+=sx(im8)
BLE <label>	0	0	1	0	0	1	0	0	im8								if N!=V or Z=1 then PC+=sx(im8)
Call & Return	<i>opcode</i>			<i>op</i>		<i>Rn</i>			<i>8b</i>								
BL <label>	0	1	0	1	1	1	1	1	im8								R7=PC; PC+=sx(im8)
BLX Rd	0	1	0	1	0	1	1	1	Rd	0	0	0	0	0	0	0	R7=PC; PC=Rd
BX Rd	0	1	0	0	0	0	0	0	Rd	0	0	0	0	0	0	0	PC=Rd

Table 5: Instructions you will add in Lab 7

- <sh_op> and sh are 2-bit immediate operands encoded as part of the instruction.
- sx(f) sign extends the immediate value f to 16-bits.
- sh_Rm is the value of Rm after passing through the shifter connected to the Bin input to the ALU.
- Z, V, and N are the zero, overflow and negative flags of the status register (only Z is implemented in Lab 5).
- status refers to all three of Z, V and N.
- R[x] refers to the 16-bit value stored in register x.
- M[x] is the 16-bit value stored in main memory (added in Lab 6) at address x.
- PC refers to the program counter register (added in Lab 6).
- <label> refers to a textual marker in the assembly that indicates an instruction address